

Opgave 4.1

$$R_{1_1} := 10\text{k}\Omega$$

$$R_{2_1} := 10\text{k}\Omega$$

$$I_{R_{2_1}} := 1\text{mA}$$

$$U_{R_{1_1}} := R_{1_1} \cdot I_{R_{2_1}} = 10\text{V}$$

$$U_{R_{2_1}} := R_{2_1} \cdot I_{R_{2_1}} = 10\text{V}$$

$$U_{cc_1} := U_{R_{2_1}} + U_{R_{1_1}} = 20\text{V}$$

Opgave 4.2

$$R_{1_2} := 1\text{k}\Omega$$

$$R_{2_2} := 1\text{k}\Omega$$

$$U_{cc_2} := 12\text{V}$$

$$R_{12_2} := R_{1_2} + R_{2_2}$$

$$I_{R_{2_2}} := \frac{U_{cc_2}}{R_{12_2}} = 6\text{mA}$$

Opgave 4.3

$$P_{R_{1_1}} := U_{R_{1_1}} \cdot I_{R_{2_1}} = 10\text{mW}$$

$$P_{R_{2_1}} := U_{R_{2_1}} \cdot I_{R_{2_1}} = 10\text{mW}$$

$$P_{R_{1_2}} := I_{R_{2_2}}^2 \cdot R_{1_2} = 36\text{mW}$$

$$P_{R_{2_2}} := I_{R_{2_2}}^2 \cdot R_{2_2} = 36\text{mW}$$

Fig. 4

